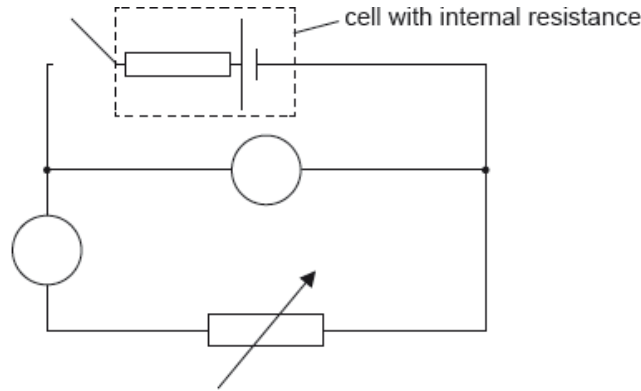



# SL Paper 3

The circuit shown may be used to measure the internal resistance of a cell.



The ammeter used in the experiment in (b) is an analogue meter. The student takes measurements without checking for a “zero error” on the ammeter.

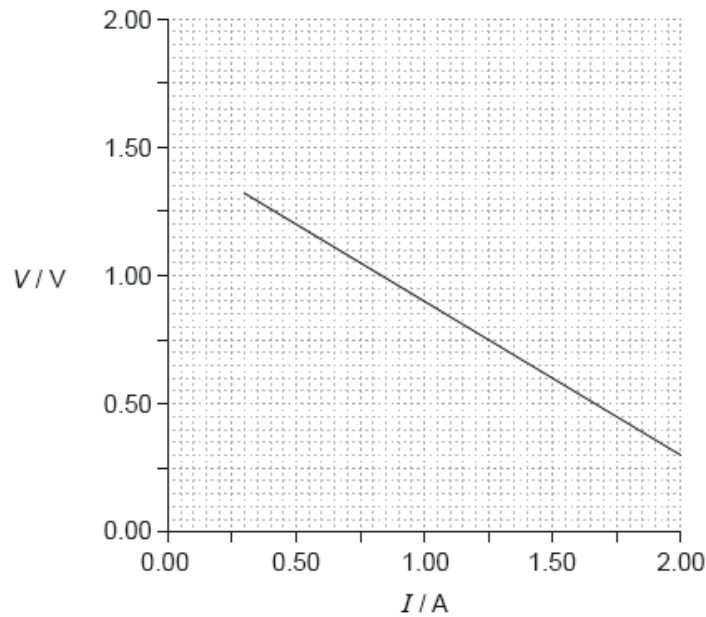
- a. An ammeter and a voltmeter are connected in the circuit. Label the ammeter with the letter A and the voltmeter with the letter V. [1]
- b. In one experiment a student obtains the following graph showing the variation with current  $I$  of the potential difference  $V$  across the cell. [3]




Using the graph, determine the best estimate of the internal resistance of the cell.

- c.i. State what is meant by a zero error. [1]
- c.ii. After taking measurements the student observes that the ammeter has a positive zero error. Explain what effect, if any, this zero error will have [2]  
on the calculated value of the internal resistance in (b).

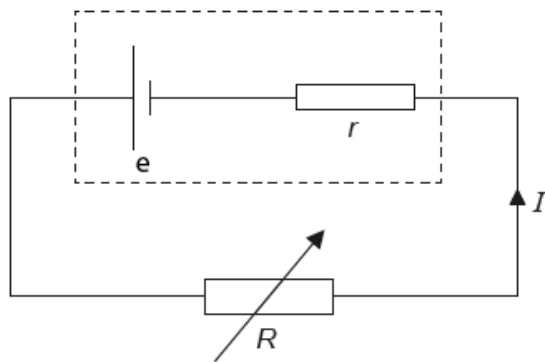An electrical circuit is used during an experiment to measure the current  $I$  in a variable resistor of resistance  $R$ . The emf of the cell is  $e$  and the cell has an internal resistance  $r$ .



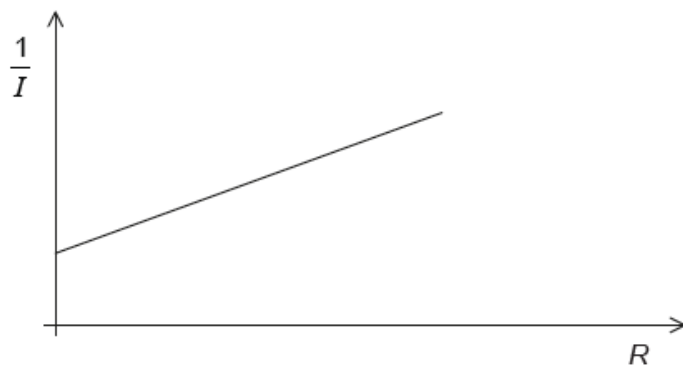A graph shows the variation of  $\frac{1}{I}$  with  $R$ .



a. Show that the gradient of the graph is equal to  $\frac{1}{e}$ .

[2]

b. State the value of the intercept on the  $R$  axis.

[1]