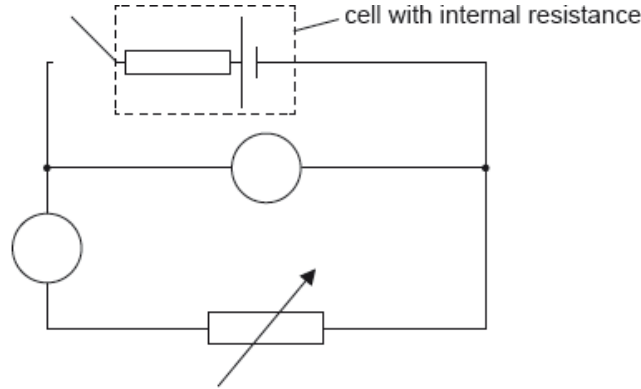



SL Paper 3

The circuit shown may be used to measure the internal resistance of a cell.



The ammeter used in the experiment in (b) is an analogue meter. The student takes measurements without checking for a “zero error” on the ammeter.

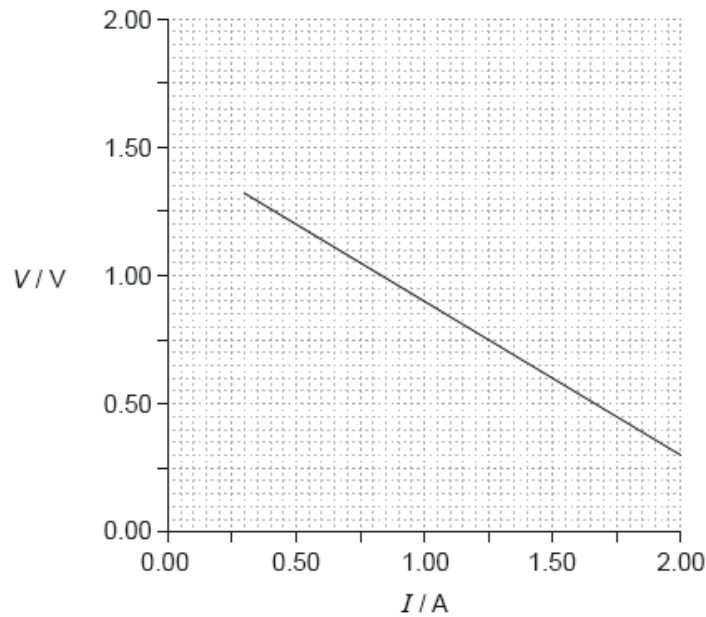- a. An ammeter and a voltmeter are connected in the circuit. Label the ammeter with the letter A and the voltmeter with the letter V. [1]
- b. In one experiment a student obtains the following graph showing the variation with current I of the potential difference V across the cell. [3]




Using the graph, determine the best estimate of the internal resistance of the cell.

- c.i. State what is meant by a zero error. [1]
- c.ii. After taking measurements the student observes that the ammeter has a positive zero error. Explain what effect, if any, this zero error will have [2]
on the calculated value of the internal resistance in (b).

Markscheme

a. correct labelling of both instruments

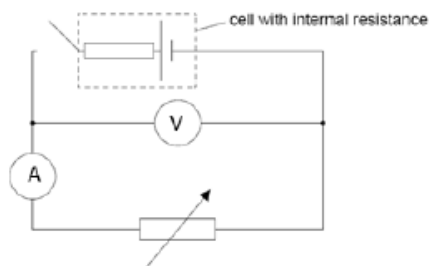

[1 mark]

b. $V = E - Ir$

large triangle to find gradient and correct read-offs from the line

OR

use of intercept $E = 1.5 \text{ V}$ and another correct data point

internal resistance = 0.60Ω

For MP1 – do not award if only $R = \frac{V}{I}$ is used.

For MP2 points at least 1 A apart must be used.

For MP3 accept final answers in the range of 0.55Ω to 0.65Ω .

[3 marks]

c.i. a non-zero reading when a zero reading is expected/no current is flowing

OR

a calibration error

OWTTE

Do not accept just “systematic error”.

[1 mark]

c.ii. the error causes «all» measurements to be high/different/incorrect

effect on calculations/gradient will cancel out

OR

effect is that value for r is unchanged

Award [1 max] for statement of “no effect” without valid argument.

OWTTE

[2 marks]

Examiners report


a. [N/A]

b. [N/A]


c.i. [N/A]

c.ii. [N/A]

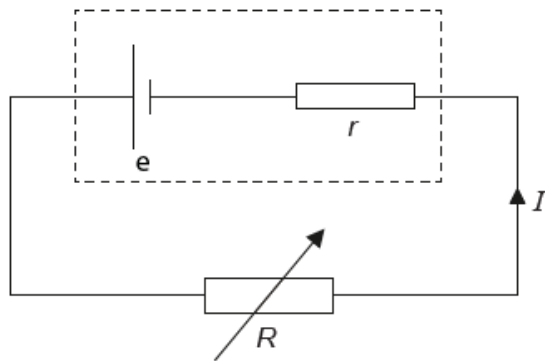An electrical circuit is used during an experiment to measure the current I in a variable resistor of resistance R . The emf of the cell is e and the cell has an internal resistance r .



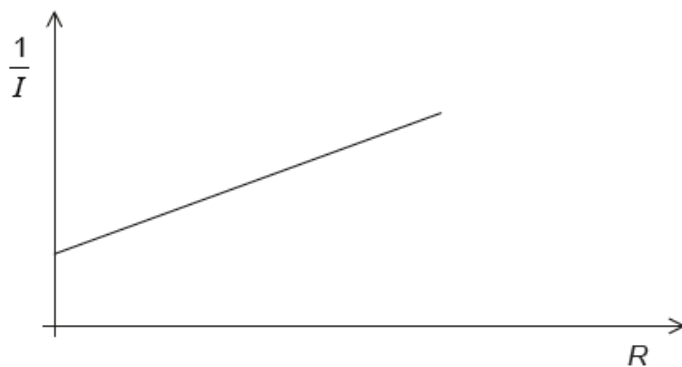A graph shows the variation of $\frac{1}{I}$ with R .



a. Show that the gradient of the graph is equal to $\frac{1}{e}$. [2]

b. State the value of the intercept on the R axis. [1]

Markscheme

a. « $\mathcal{E} = IR + Ir$ »

$$\frac{1}{I} = \frac{R}{\mathcal{E}} + \frac{r}{\mathcal{E}}$$

identifies equation with $y = mx + c$

«hence $m = \frac{1}{\mathcal{E}}$ »

No mark for stating data booklet equation

Do not accept working where r is ignored or $\mathcal{E} = IR$ is used

OWTTE

b. « \rightarrow » r

Allow answer in words

Examiners report

a. [N/A]

b. [N/A]

